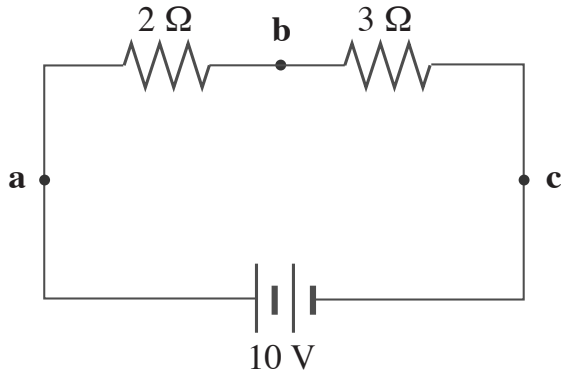



DC Circuits Practice Items

The diagram below pertains to questions 1-6.



- In what manner does current flow through the circuit?
 - clockwise
 - counter-clockwise
 - there is no current
 - alternating current
- What is the value of the current at point **a**?
 - 0 A
 - 2.0 A
 - 5.0 A
 - 8.3 A
- What is the value of the current at point **b**?
 - 0 A
 - 2.0 A
 - 5.0 A
 - 8.3 A
- What is the potential difference between points **b** and **c**?
 - 6 V
 - 2 V
 - 6 V
 - 10 V
- What is the potential difference between points **c** and **a**?
 - 10 V
 - 2 V
 - 2 V
 - 10 V
- If the two resistors in the circuit are heating elements submerged in 0.5 liters of water, approximately how long would it take to raise the temperature $1\ ^\circ\text{C}$?
 - 25 seconds
 - 0.5 seconds
 - almost two minutes
 - about two hours

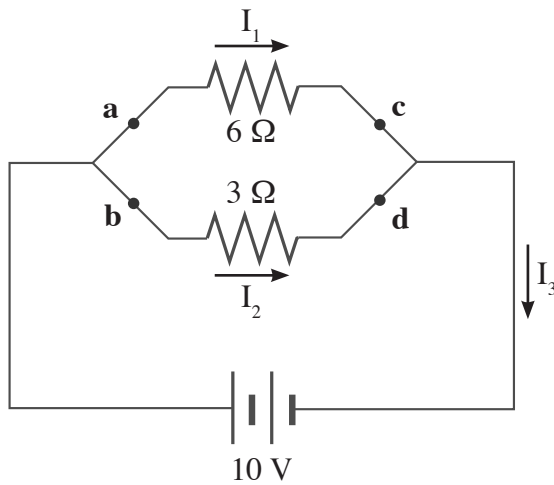The diagram below pertains to questions 7 - 12.



7. In the circuit pictured above, what is the potential difference between points **b** and **c**?

- A. - 10 V
- B. - 3.3 V
- C. 3.3 V
- D. 10 V

8. What is the value of I_3 ?

- A. 1.1 A
- B. 3.3 A
- C. 5 A
- D. 20 A

9. What is the value of I_2 ?

- A. 1.1 A
- B. 3.3 A
- C. 5 A
- D. 20 A

10. What is the value of the power consumption of the entire circuit?

- A. 2.0 W
- B. 10 W
- C. 20 W
- D. 50 W


11. Assuming the power supply remained unchanged in delivering 10V to the external circuit, if the wire were cut at point **b**, which of the following would occur?

- A. I_1 would increase
- B. I_1 would decrease
- C. I_2 would increase
- D. I_3 would decrease

12. Which of the following statements is **untrue**?

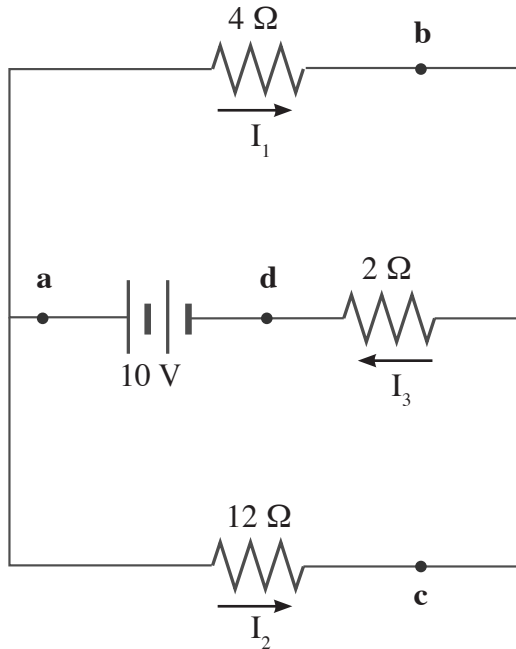
- A. I_2 is twice the value of I_1
- B. $I_1 + I_2 = I_3$
- C. The power consumption of the 6 Ω resistor is equal to the power consumption of the 3 Ω resistor.
- D. all are true

The diagram below pertains to questions 13 - 15.



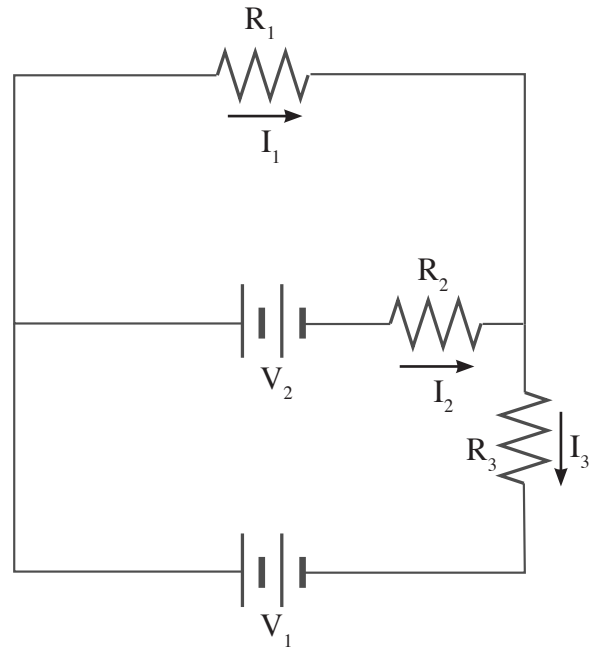
13. What is the value of I_3 ?
- 0.63 A
 - 2.0 A
 - 3.3 A
 - 8.3 A
14. What is the value of the power consumed by the 12 Ω resistor?
- 6 W
 - 3 W
 - 72 W
 - $25/3$ W
15. Which of the following statements is **untrue**?
- The potential difference between points b and c is zero.
 - I_1 is greater than I_2 .
 - The potential difference between points b and d is 10 V.
 - All are true.

The diagram below pertains to questions 16 - 17.



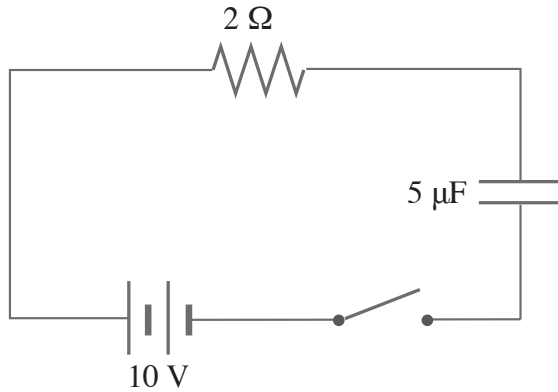16. Which of the following expressions is incorrect?
- $V_1 - I_1 R_1 - I_3 R_3 = 0$
 - $V_1 - V_2 - I_2 R_2 - I_3 R_3 = 0$
 - $I_1 + I_2 = I_3$
 - all are correct
17. If instead of the voltage source, V_2 , a fully charged capacitor were present at that same position in the circuit, which of the following would occur?
- I_1 would equal I_3 .
 - The rest of the circuit would attain a net positive charge.
 - I_1 would be greater than I_3 .
 - The voltage drop across the capacitor would be equal and opposite to V_1 .

The diagram below pertains to questions 18 - 20.



18. In the RC circuit above, what is the maximum rate of power consumption by the resistor?
- A. 5 W
 - B. 25 W
 - C. 50 W
 - D. 100 W
19. When the capacitor has been fully charged, how much charge will it hold?
- A. $50\ \mu\text{C}$
 - B. 50 mC
 - C. 2.0 C
 - D. $2.0 \times 10^6\ \text{C}$
20. Which of the following statements predicts the behavior of the circuit?
- A. Immediately after the switch has been closed, the potential drop will be entirely across the resistor.
 - B. After the capacitor has been fully charged, the potential drop will be entirely across the capacitor.
 - C. Employing a dielectric within the capacitor will increase the amount of charge stored in the fully charged capacitor.
 - D. all of the above



© 2020 Wisebridge Learning Systems LLC. Some rights reserved. This work is published under a Creative Commons Attribution Non-Commercial ShareAlike License.

www.integrated-mcat.com

